 


# Examen 1 : Diseño de Sistemas Digitales


Profesor: Alexis Testa Nava

Alumno: Ramírez Cotonieto Luis Fernando

Con base en el siguiente circuito, resuelva lo que se pide.




 
1.- Realice el cronograma de tiempos correspondiente al diagrama lógico de la Fig.1



2.- Realice el circuito en Falstad y simule el correcto funcionamiento.  
(adjuntar el link y capturas de pantalla del circuito realizado, individual).

<https://tinyurl.com/ye3zmqpx>

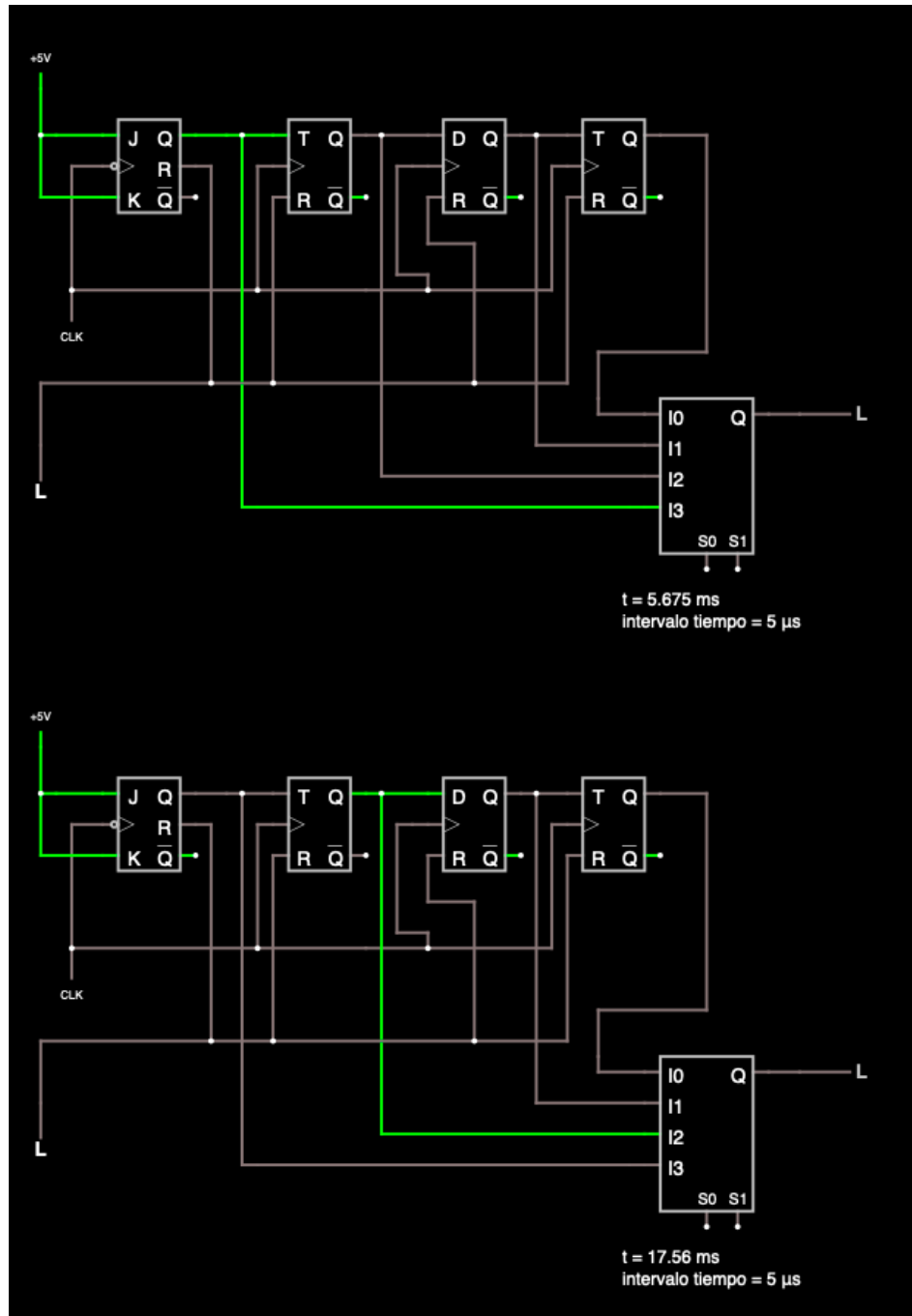

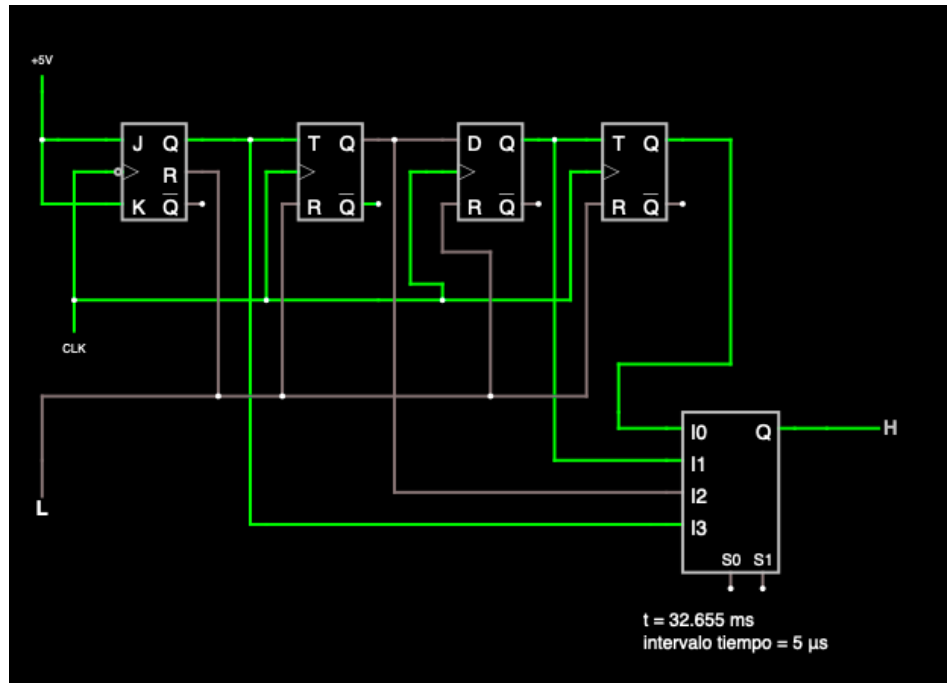

3.- Diseñar el circuito en HDL funcional (adjuntar código VHD en txt. Capturas del código, compilación y simulaciones)

```
library ieee;
use ieee.std_logic_1164.all;

-----FLIP-FLOPS-----

-----FLIP-FLOP-D-----

entity FFTD is port(
    D,clear,preset,clock:in std_logic;
    Q,Qnot: inout std_logic
);
end FFTD;

architecture funcional of FFTD is
begin
    process (clear,preset,clock)
    begin
        if preset='1' then
            Q<= '1';
```

```

        Qnot<='0';
    elsif clear = '1' then
        Q<= '0';
        Qnot<='1';
    elsif (clock'event and clock='1') then
        Q<= D;
        Qnot<= not D;
    end if;
end process;
end architecture;

```

#### -----FLIP-FLOP-JK-----

```

entity FFTJK is port(J,K,clear,preset,clock:in std_logic;
    Q,Qnot: inout std_logic
);
end FFTJK;

```

architecture funcional of FFTJK is

```

begin
    process (clear,preset,clock)
    begin
        if preset='1' then
            Q<= '1';
            Qnot<= '0';
        elsif clear = '1' then
            Q<= '0';
            Qnot<='1';
        elsif (clock'event and clock='1') then
            if (J='0' and K='0') then
                Q<=Q;
                Qnot<=Qnot;
            elsif(J='1' and K='0')then
                Q<='1';
                Qnot<='0';
            end if;
        end if;
    end process;
end funcional;

```

```

        elsif (J='0' and K='1')then
            Q<='0';
            Qnot<='1';
        elsif (J='1' and K='1')then
            Q<=Qnot;
            Qnot<=Q;
        end if;
    end if;
end process;
end architecture;

```

#### -----FLIP-FLOP-T-----

```

entity FFTT is port(
    T,clear,preset,clock:in std_logic;
    Q,Qnot: inout std_logic
);
end FFTT;

```

architecture funcional of FFTT is

```

begin
    process (clear,preset,clock)
    begin
        if preset='1' then
            Q<= '1';
            Qnot<= '0';
        elsif clear = '1' then
            Q<= '0';
            Qnot<='1';
        elsif (clock'event and clock='1') then
            if T='0' then
                Q<=Q;
                Qnot<=Qnot;
            elsif T = '1' then
                Q<= Qnot;
                Qnot<= Q;
            end if;
        end if;
    end process;
end funcional;

```

```

        end if;
    end if;
end process;
end architecture;

```

#### -----MUX-----

```

entity MUX is port(
    a,b,c,d,s0,s1: in std_logic;
    y: out std_logic
);
end MUX;

```

```

architecture combinational of MUX is
    signal x0,x1,x2,x3: std_logic;
begin
    x0<= a and (not s0) and (not s1);
    x1<= b and (not s1) and s0;
    x2<= c and s1 and (not s0);
    x3<= d and s0 and s1;
    y<= x0 or x1 or x2 or x3;
end architecture;

```

#### -----EXAMEN PRIMER PARCIAL-----

```

use work.all;
architecture estructural of PrimPar is
    component FFTJK
    is port(
        J,K,clear,preset,clock:in std_logic;
        Q,Qnot: inout std_logic
    );
    end component;
    component FFTD is port(
        D,clear,preset,clock:in std_logic;
        Q,Qnot: inout std_logic
    );
    end component;

```

```

    component FFTT
is port(
    T,clear,preset,clock:in std_logic;
    Q,Qnot: inout std_logic
);
end component;
    component MUX is port(
    a,b,c,d,s0,s1: in std_logic;
    y: out std_logic
);
end component;
    signal Q1,Q2,Q3,Q4: std_logic;
begin
    FFJK: FFTJK
port map(
    J=>J,K=>K,clear=>clear,preset=>'0',clock=>clk,Q=>Q1
);
    FFT1: FFTT
port map(
    T=>Q1,clear=>clear,preset=>'0',clock=>clk,Q=>Q2
);
    FFTD: FFTD port map(
    D=>Q2, clear=>clear,preset=>'0',clock=>clk,Q=>Q3
);
    FFT2: FFTT
port map(
    T=>Q3,clear=>clear, preset=>'0',clock=>clk,Q=>Q4
);
    MUX: MUX port map(
    a=>Q1, b=> Q2, c=>Q3, d=>Q4, s0=>s0,s1=>s1, y=>Q
);

end architecture;

```